

Please check that this question paper contains 9 questions and 2 printed pages within first ten minutes.

MORNING

[Total No. of Questions: 09]

24 JUN 2023

[Total No. of Pages: 2]

Uni. Roll No. ....

Program: B.Tech. (Batch 2018 onward)

Semester: 3

Name of Subject: Electronic Devices

Subject Code: PCEC-101

Paper ID: 16031

Scientific calculator is Allowed

Time Allowed: 03 Hours

Max. Marks: 60

NOTE:

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

Part – A

[Marks: 02 each]

Q1.

- a) Define diffusion.
- b) Justify, the need of operating point.
- c) Define pinch off voltage for FET.
- d) Write the significance of alpha cut off frequency.
- e) Compare LED and LCD.
- f) Distinguish enhancement and depletion MOSFET.

Part – B

[Marks: 04 each]

- Q2. Discuss various energy bands in a semiconductor.
- Q3. Describe theory of PN junction diode.
- Q4. Explain the operation and characteristics of Unijunction Transistor (UJT).
- Q5. Derive an expression for efficiency of half-wave rectifier.
- Q6. Illustrate h-parameter equivalent circuit of transistor to discuss meaning of h-parameters.
- Q7. Compare intrinsic and extrinsic silicon.

Part – C

[Marks: 12 each]

- Q8. Explain construction and working of NPN transistor. Also discuss input and output characteristics of NPN transistor in common emitter configuration.

Page 1 of 2

P.T.O.

MORNING

24 JUN 2023

OR

Discuss the following:

(a) Tunnel diode

(b) Generation and recombination of carriers in a semiconductor

Q9. (a) Create and explain drain characteristics curve of JFET.

(b) An N-channel JFET has  $I_{DSS}=10$  mA and  $V_p = -4$ V. Determine the minimum value of  $V_{DS}$  for pinch-off region and drain current  $I_D$  for  $V_{GS} = -2$ V in pinch-off region.

OR

Derive an expression for input impedance, output impedance, voltage gain and current gain using analysis of Common base transistor amplifier using h-parameters.

\*\*\*\*\*